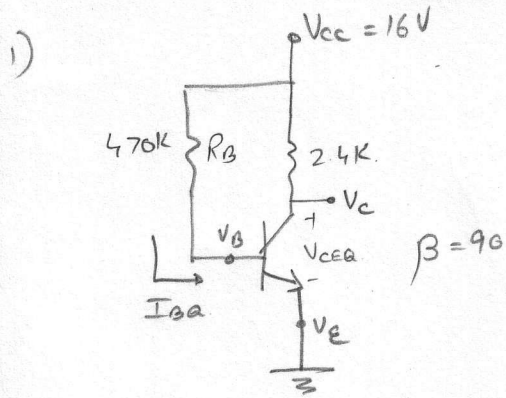


PS#5
SOLUTIONS



a) $V_{CC} = I_B R_B + V_{BE}$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$= \frac{16 - 0.7}{470K}$$

$$I_{BQ} = 32.6 \mu A$$

b) $I_{CQ} = \beta I_{BQ}$

$$I_{CQ} = 2.93 mA$$

c) $V_{CEQ} = V_{CC} - I_C R_C$

$$V_{CEQ} = 8.08V$$

d) $V_{CE} = V_C - V_E$

Here $V_E = 0$

$$\therefore V_{CE} = V_C$$

$$\therefore V_C = 8.08V$$

e) $V_{BE} = V_B - V_E$

$$\therefore V_B = 0.7V$$

$$\therefore V_E = 0$$

f) $V_E = 0V$