

Problem set #6 - Part 1

1

1

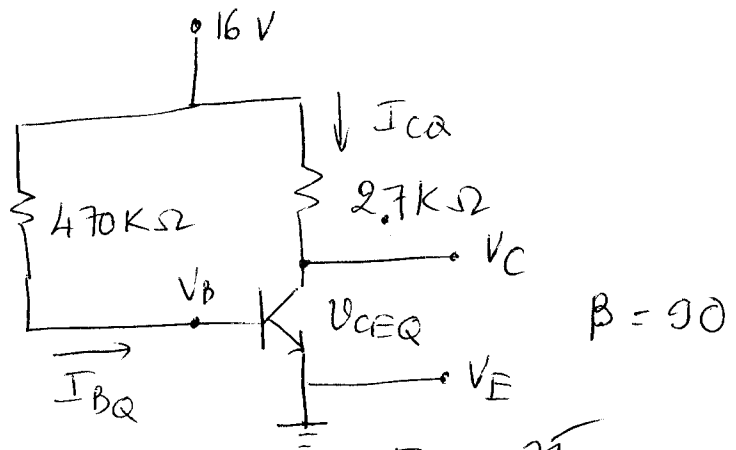


Fig 4.73

a) Find I_{BQ} :

$$16 = 470\text{k}\Omega \cdot I_{BQ} + V_{BE} \rightarrow 0.7$$

$$\Rightarrow I_{BQ} = \frac{16 - 0.7}{470\text{k}\Omega} = \boxed{32.6 \mu\text{A}} \checkmark$$

b) $I_{CQ} = ?$

$$I_{CQ} = \beta I_{BQ} = 90 \cdot 32.6 \mu\text{A} = 2.93 \text{ mA}$$

$$I_{C\text{max}} = \frac{16 - 0.2}{2.7\text{k}\Omega} = 5.85 \text{ mA}$$

$$\Rightarrow I_{CQ} < I_{C\text{max}} \Rightarrow \boxed{I_{CQ} = 2.93 \text{ mA}} \checkmark \text{ (A.F. region)}$$

c) $V_{CEQ} = ?$

$$V_{CEQ} = 16 \text{ V} - 2.7\text{k}\Omega \cdot I_{CQ}$$

$$V_{CEQ} = 16 \text{ V} - 2.7\text{k}\Omega \cdot 2.93 \text{ mA}$$

$$\boxed{V_{CEQ} \approx 8.09 \text{ V}} \checkmark$$

d) $V_C = ?$

$$V_C = V_{CEQ} = \boxed{8.09 \text{ V}} \checkmark$$

e) $V_B = V_{BE} = \boxed{0.7 \text{ V}} \checkmark$

f) $\boxed{V_E = 0 \text{ V}} \checkmark$

Problem Set # 6 - Part 1

(2)

- 4) Find saturation current I_C for the fixed bias configuration of Fig 4.75

$$I_{Cmax} = \frac{16V - 0.2V}{2.7K\Omega} = 5.85mA$$

6)

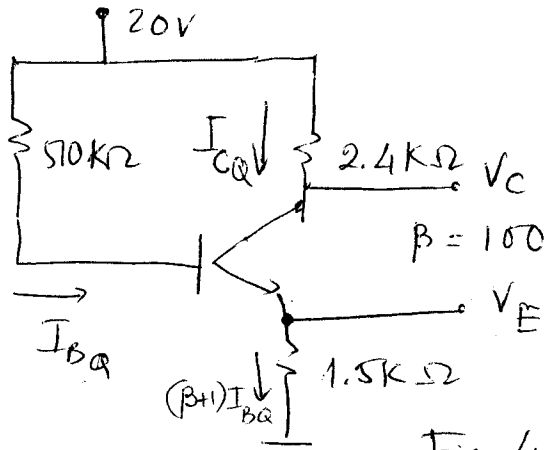


Fig 4.79

- a) Find I_{BQ} ?

$$20V = 510K\Omega \times I_{BQ} + V_{BE} + 1.5K\Omega \cdot (\beta+1)I_{BQ}$$

$$\Rightarrow I_{BQ} (510K\Omega + 1.5K\Omega \times 101) = 20 - 0.7$$

$$\Rightarrow I_{BQ} = \frac{20 - 0.7}{510K\Omega + 151.5K\Omega} = \boxed{29.2 \mu A}$$

- b) $I_{CQ} = ?$

$$I_{CQ} = \beta I_{BQ} = 29.2 \mu A \times 100 = 2.92 mA$$

$$I_{Cmax} = \frac{20V - 0.2V}{2.4K\Omega + \left(\frac{\beta+1}{\beta}\right) \cdot 1.5K\Omega} \approx \frac{19.8V}{3.9K\Omega} = 5.07mA$$

$$\Rightarrow I_{CQ} < I_{Cmax} \Rightarrow \boxed{I_{CQ} = 2.92mA} \text{ (Active region)}$$

- c) $V_{CEQ} = ?$

$$V_{CEQ} = 20V - 2.4K\Omega \times I_{CQ} - \left(\frac{\beta+1}{\beta}\right) I_{CQ} \cdot 1.5K\Omega$$

$$V_{CEQ} = 20V - 2.4K\Omega \times 2.92mA - \frac{101}{100} \cdot 2.92 \times 1.5K\Omega$$

$$\boxed{V_{CEQ} = 8.56V}$$

Problem set # 6 - Part 1

⑥ (cont.)

d) $V_C = ?$

$$V_C = V_{CEQ} + 1.5K\Omega \times \frac{\beta+1}{\beta} \cdot I_C$$

$$V_C = 8.56 + 1.5K\Omega \times \frac{100}{100} \cdot 2.92$$

$$V_C = 12.98 V$$

e) $V_B = ?$

$$V_B = V_{BE} + V_E = 0.7 + \frac{\beta+1}{\beta} \cdot 1.5K\Omega \cdot I_{CQ}$$

$$V_B = 0.7 + \frac{100}{100} \times 1.5K\Omega \times 2.92 \Rightarrow$$

$$V_B = 5.12 V$$

f) $V_E = ?$


$$V_E = \frac{\beta+1}{\beta} \cdot I_{CQ} \cdot 1.5K\Omega$$

$$V_E = 4.42 V$$

Problem set #6 Part 1

(4)

(11)

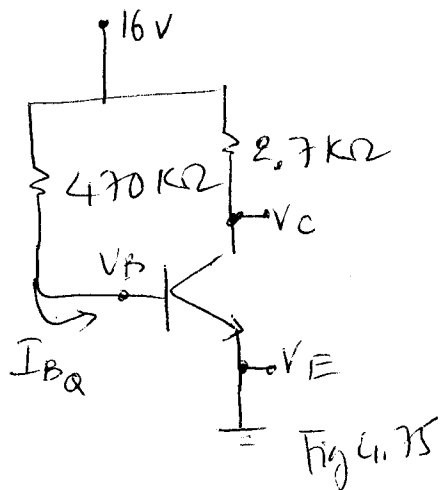

a) $I_C \propto V_{CE} = ?$

$\beta = 90 \Rightarrow$

$I_C = 2.93 \text{ mA}$

$V_{CE} = 8.09 \text{ V}$

Did in page 4

See solution Problem Set #6 Part 1 - page 1

b) $\beta = 135$ $I_C, V_{CE} = ?$

$I_{C \text{ max}} = \frac{16 - 0.2}{2.7} = 5.85 \text{ mA}$; $I_{BQ} = 32.6 \mu\text{A}$ (see page 1)

$I_{CQ} = \beta I_{BQ} = 135 \times 32.6 \mu\text{A} = 4.4 \text{ mA}$ ✓

$I_{CQ} < I_{C \text{ max}} \Rightarrow I_{CQ} = 4.4 \text{ mA}$ (A.F region)

$V_{CE} = 16 \text{ V} - 2.7 \text{ k}\Omega \cdot I_{CQ} = 16 - 2.7 \times 4.4$

$V_{CE} = 4.12 \text{ V}$ ✓

c) $\% \Delta I_C = \left| \frac{I_{C \text{ part b}} - I_C}{I_{C \text{ max a}}} \right| \times 100\% = \left| \frac{4.4 - 2.93}{2.93} \right| \times 100\% = 50\%$ ✓

$\% \Delta V_{CE} = \left| \frac{V_{CE(b)} - V_{CE(a)}}{V_{CE(a)}} \right| \times 100\% = \left| \frac{4.12 - 8.09}{8.09} \right| \times 100\% = 49\%$ ✓

d) Fig 4.79 $\rightarrow I_C$ and $V_{CE} ?$

$I_{CQ} = 2.92 \text{ mA}$

$V_{CEQ} = 8.56 \text{ V}$

e) Change $\beta = 150$, $I_C, V_{CE} ?$ of Fig. 4.79

$I_{C \text{ max}} = \frac{20 \text{ V} - 0.2 \text{ V}}{2.7 \text{ k}\Omega} = 5.07 \text{ mA}$

$I_{BQ} = \frac{V_{CC} - 0.7}{\frac{2.4 \text{ k}\Omega}{150} + 1.5 \text{ k}\Omega} = 0.026 \text{ mA}$

$I_{CQ} = \beta I_{BQ} = 150 \times 0.026 \text{ mA} = 3.93 \text{ mA}$ ✓

$I_{CQ} < I_{C \text{ max}} \Rightarrow$ Active F. region $\Rightarrow I_{CQ} = 3.93 \text{ mA}$ ✓

$$e) I_{CQ} = 3.93 \text{ mA}$$

$$V_{CEQ} = 20 \text{ V} - 3.93 \times (2.4 + 1.5) = \boxed{4.67 \text{ V}}$$

$$f) \% \Delta I_C = \left| \frac{I_{C(e)} - I_{C(d)}}{I_{C(d)}} \right| = \left| \frac{3.93 - 2.92}{2.92} \right| \times 100\% = \boxed{34.6\%}$$

$$\% \Delta V_{CE} = \left| \frac{V_{CE(e)} - V_{CE(d)}}{V_{CE(d)}} \right| = \left| \frac{4.67 - 8.56}{8.56} \right| \times 100\% = \boxed{45.4\%}$$



g) Fig 4.75	$\% \Delta I_C = 50\%$	$\% \Delta V_{CE} = 49\%$
Fig 4.79	$\% \Delta I_C = 34.6\%$	$\% \Delta V_{CE} = 45.4\%$

The circuit in Fig 4.79 seems to be less sensitive to changes in β .

Problem Set # 6 - Part 1

6

12

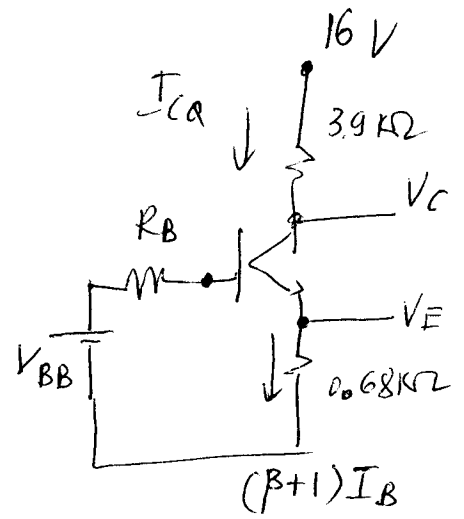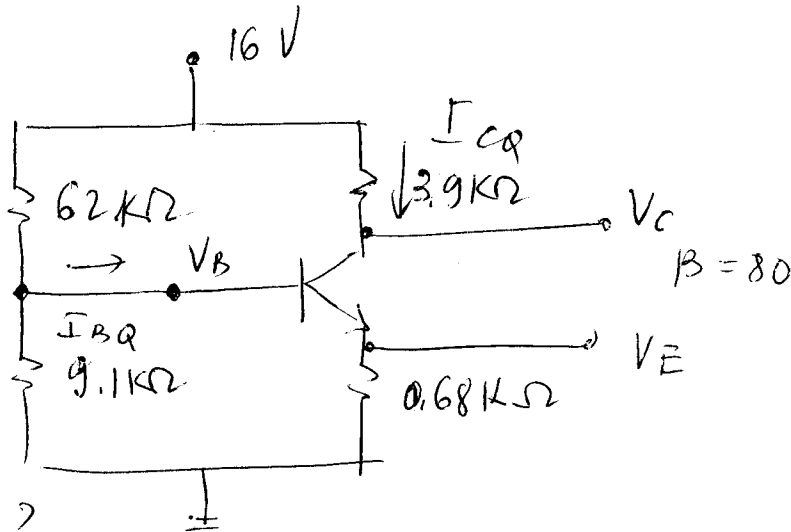

a) $I_{BQ} = ?$
 $V_{BB} = \frac{16V \cdot 9.1k\Omega}{62k\Omega + 9.1k\Omega} = 2.05V$

$R_B = 62k\Omega \parallel 9.1k\Omega = \frac{62 \times 9.1}{62 + 9.1} = 7.93k\Omega$

$I_{BQ} = \frac{V_{BB} - 0.7}{R_B + (\beta + 1)R_E} = \frac{2.05V - 0.7}{7.93k\Omega + 81 \times 0.68k\Omega} = \boxed{21.4\mu A} \checkmark$

b) $I_{CQ} = ?$
 $I_{Cmax} = \frac{16V - 0.2}{3.9k\Omega + 0.68k\Omega} = 3.45mA$

$I_{CQ} = \beta I_{BQ} = 80 \times 21.4\mu A = 1.71mA < I_{Cmax}$
 $\Rightarrow \boxed{I_{CQ} = 1.71mA} \checkmark$ (Active F. region)


c) $V_{CEQ} = ?$
 $V_{CEQ} = 16V - I_{CQ} (3.9k\Omega + 0.68k\Omega) \checkmark$
 $V_{CEQ} = 16V - 1.71 (4.58)k\Omega = \boxed{8.17V} \checkmark$

d) $V_C = ?$
 $V_C = 16V - 3.9k\Omega \times 1.71 = \boxed{9.33V} \checkmark$

e) $V_E = ?$
 $V_E = I_{CQ} \left(\frac{\beta + 1}{\beta} \right) \cdot 0.68k\Omega = 1.71 \times 0.68 = \boxed{1.16V} \checkmark$

f) $V_B = V_E + 0.7 = 1.16 + 0.7 = \boxed{1.86V} \checkmark$

14

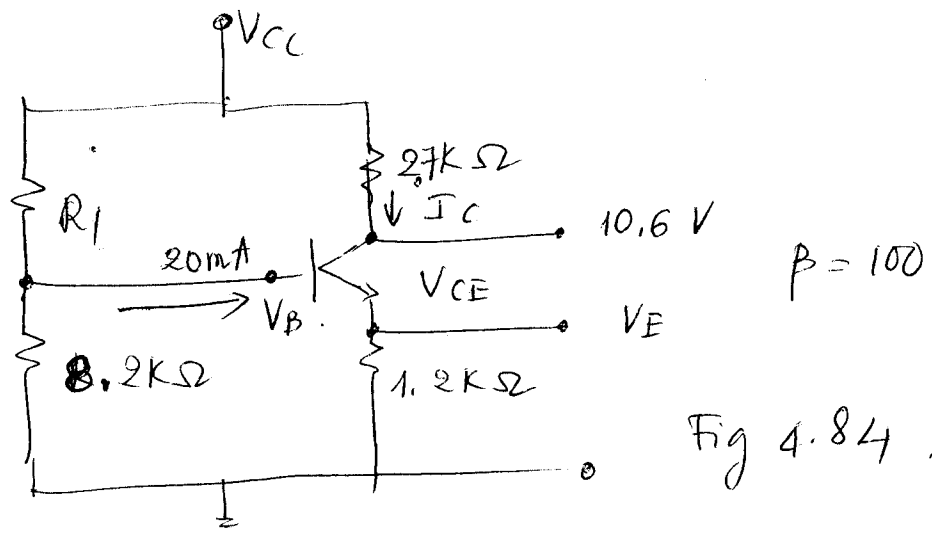

a) $I_C = ?$ given
 We have $I_{BQ} = 20 \mu A \Rightarrow I_{CQ} = \beta I_{BQ} = 100 \times 20 \mu A = \boxed{2 \text{ mA}}$

b) $V_E = ?$
 $V_E = \frac{(\beta + 1) I_{BQ} \cdot 1.2 \text{ k}\Omega}{\beta} = (101) \cdot 20 \mu A \cdot 1.2 \text{ k}\Omega = \boxed{2.42 \text{ V}}$

c) $V_{CC} = ?$ given
 $V_{CC} = 2.7 \text{ k}\Omega I_{CQ} + 10.6 \text{ V}$
 $\Rightarrow V_{CC} = 2.7 \text{ k}\Omega \cdot 2 \text{ mA} + 10.6 \text{ V} = \boxed{16 \text{ V}}$

d) $V_{CE} = ?$
 $V_{CE} = 10.6 \text{ V} - V_E = 10.6 \text{ V} - 2.42 \text{ V}$
 $\boxed{V_{CE} = 8.18 \text{ V}}$

e) $V_B = 0.7 + V_E = 0.7 \text{ V} + 2.42 \text{ V} = \boxed{3.12 \text{ V}}$
 $V_{BB} = \frac{V_{CC} \cdot 8.2}{R_1 + 8.2 \text{ k}\Omega} > 16 \text{ V}$

f) $R_1 = ?$
 $R_B = \frac{R_1 \cdot 8.2 \text{ k}\Omega}{R_1 + 8.2 \text{ k}\Omega}$
 $V_{BB} = R_B \cdot 20 \mu A + V_B$
 $\frac{16 \times 8.2}{R_1 + 8.2} = \frac{R_1 \cdot 8.2}{R_1 + 8.2} \times \frac{20 \times 10^{-3}}{\text{mA}} + 3.12 \text{ V}$
 $(3.12 R_1 + 0.164 R_1) = 16 \times 8.2 - 25.58$
 $\Rightarrow \boxed{R_1 = 32.16 \text{ k}\Omega}$