


PROBLEM 2

BJT dc Large Signal Model--Fixed Biasing

The dc bias circuit shown has $V_{CC} = 15\text{ V}$, $R_B = 200\text{ k}\Omega$, $R_C = 1\text{ k}\Omega$,
For the following two cases determine whether the transistor is in active region or in saturation, and solve for I_C , and V_{CE}

CASE A) $\beta = 100$

CASE B) $\beta = 300$.

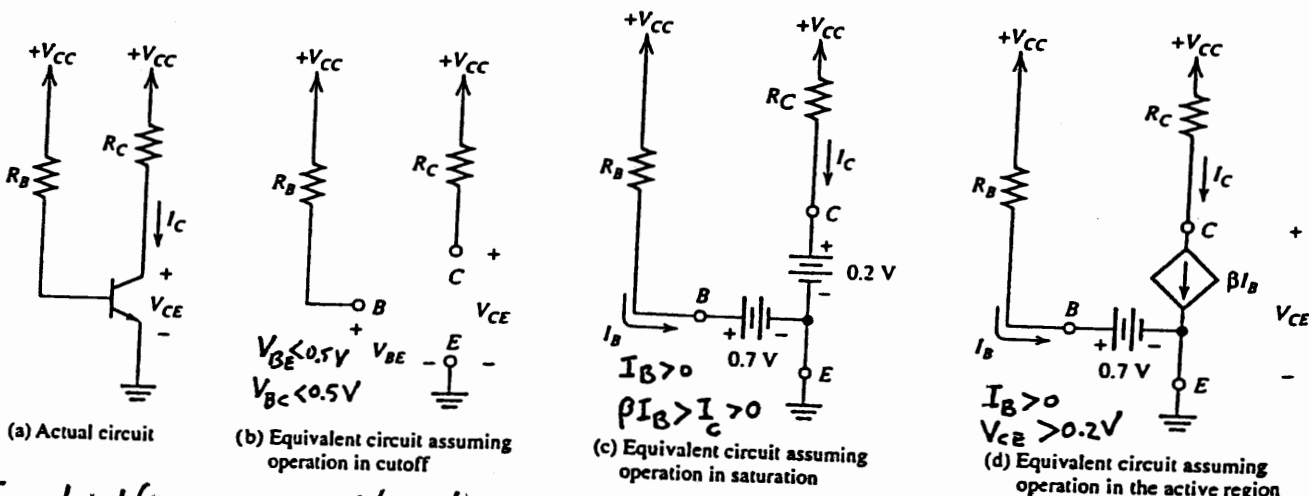

In both cases, the transistor cannot be in cutoff or Reverse Active (since $V_{CC} > 0$) So we must examine two possibilities in each case: Saturation or Forward Active.

1) Assume Saturation then use circuit (c). Find I_B and I_C

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} \Rightarrow I_B = \frac{15 - 0.7}{200} \frac{\text{V}}{\text{k}\Omega} = 71.5 \mu\text{A}$$

$$I_C = \frac{V_{CC} - V_{CE}}{R_C} \Rightarrow I_C = \frac{15 - 0.2}{1} \frac{\text{V}}{\text{k}\Omega} = 14.8 \text{ mA}$$

Now Test $\frac{I_C}{I_B} = \frac{14.8 (\text{mA})}{71.5 (\mu\text{A})} \approx 270 \therefore 100 < \frac{I_C}{I_B} < 300$

CONCLUSION: For $\beta = 100$ $\frac{I_C}{I_B} > \beta \Rightarrow$ assumption of Saturation is Wrong.

For $\beta = 300$ $\frac{I_C}{I_B} < \beta \Rightarrow$ Saturation is INDEED CORRECT

\therefore For $\beta = 300$ Transistor is Saturated with $I_B = 71.5 \mu\text{A}$, $I_C = 14.8 \text{ mA}$, $V_{CE} = 0.2\text{V}$

For $\beta = 100$ Transistor is NOT saturated then it must be in forward Active Region. To solve we must use circuit (d)

P.T.O. \rightarrow

PROBLEM 2 continued


$\beta = 100 \Rightarrow$ Forward Active

$$I_B = \frac{15 - 0.7}{220} \frac{V}{k\Omega} = 71.5 \mu A \text{ As before}$$

$$I_C = 100 I_B = 7.15 \text{ mA}$$

$$V_{CE} = 15 - 7.15 \times 1 \text{ (mA} \times k\Omega)$$

$$V_{CE} = 7.85 \text{ V}$$

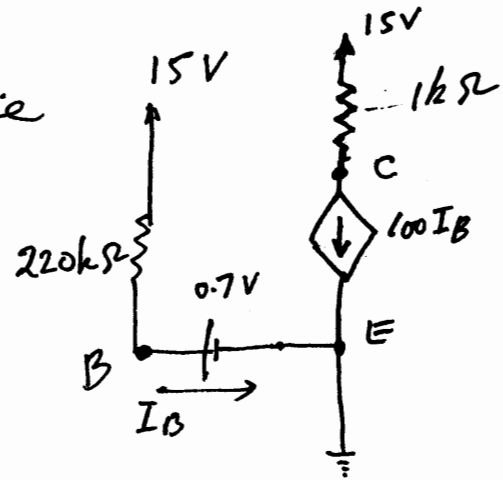

OBSERVATION

It was less time consuming to:

- 1) Treat the problem as 1
- 2) It's easier to assume saturation = first

Don't forget here the test criteria is

Simple: If $\frac{I_C}{I_B} < \beta$ Then assumption

is correct If $\frac{I_C}{I_B} > \beta$ " "

is wrong \rightarrow Forward Active