
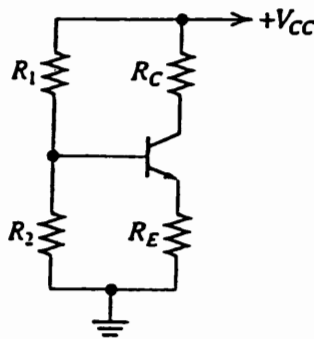


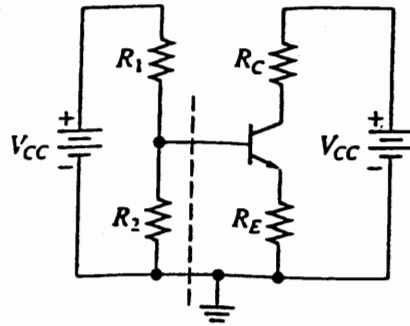PROBLEM 3


BJT dc Large Signal Model--Four Resistor Biasing



(a) Original circuit



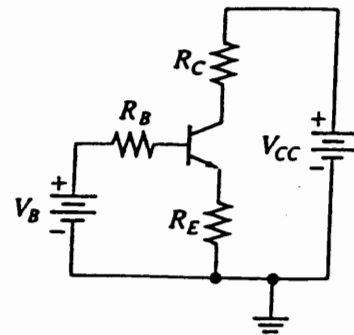
(b) Equivalent showing separate voltage sources for base and collector circuits



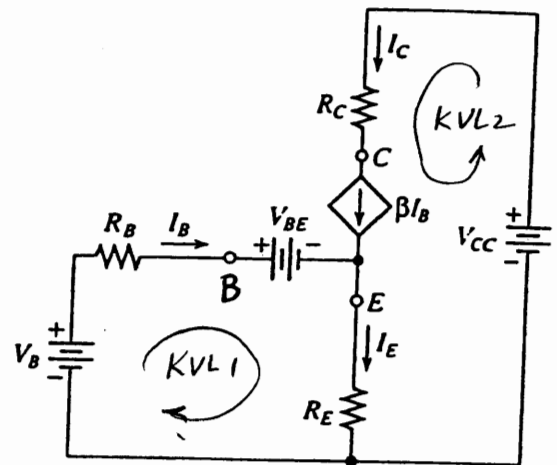(c) Circuit using Thévenin equivalent in place of VCC, R1, and R2

Consider the ideal BJT in a Four-resistor (voltage divider) bias configuration. Assume BJT is operating in active region. Refer to figures and in explicit and clear steps obtain expressions for the following in terms of V_{BE} , V_{CC} , R_1 , R_2 , R_C , R_E , and β :

- V_B
- R_B
- I_B
- I_E
- Slope and intersection of the dc load line with the V_{CE} and I_C axes.



(d) Equivalent to part (c) with active-region transistor model

a) V_B is the Thevenin voltage of the left circuit in figure (b)

$$V_B = V_{oc} = \frac{R_2}{R_1 + R_2} V_{CC}$$

b) R_B is the Thevenin resistance for same circuit

$$R_B = \frac{R_2 R_1}{R_1 + R_2}$$

c) Using Circuit (d) $R_B I_B + V_{BE} + R_E I_E - V_B = 0$ (KVL1) }
 KCL $\Rightarrow I_E = I_C + I_B$ }
 $I_E = (\beta + 1) I_B$ }

Substituting for $I_E \Rightarrow$

$$R_B I_B + V_{BE} + R_E (\beta + 1) I_B - V_B = 0$$

$$\therefore I_B = \frac{V_B - V_{BE}}{R_B + (\beta + 1) R_E}$$

$$\text{OR } I_B = \frac{\left(\frac{R_2}{R_1 + R_2}\right) V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E}$$

PROBLEM 3 continued

$$d) I_E = (\beta + 1) I_B$$

$$\therefore I_E = (\beta + 1) \frac{V_B - V_{BE}}{R_B + (\beta + 1) R_E} \quad \text{OR} \quad I_E = (\beta + 1) \frac{\left(\frac{R_2}{R_1 + R_2}\right) V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E}$$

$$\text{OR} \quad I_E = \frac{V_B - V_{BE}}{\left(\frac{1}{\beta + 1}\right) R_B + R_E}$$

$$\text{OR} \quad I_E = \frac{\left(\frac{R_2}{R_1 + R_2}\right) V_{CC} - V_{BE}}{\frac{1}{(\beta + 1)} R_B + R_E}$$

$$e) \text{ KVL}_2: R_C I_C + V_{CE} + R_E I_E = V_{CC}$$

$$I_E = (\beta + 1) I_B \Rightarrow I_E = \frac{(\beta + 1)}{\beta} I_C$$

$$\therefore \text{KVL}_2 \Rightarrow \left(R_C + \left(\frac{\beta + 1}{\beta}\right) R_E \right) I_C = V_{CC} - V_{CE}$$

$$\therefore I_C = \frac{V_{CC} - V_{CE}}{R_C + \left(\frac{\beta + 1}{\beta}\right) R_E} \quad \text{Load line Eq.}$$

$$I_C = \underbrace{\left[-\frac{1}{R_C + \left(\frac{\beta + 1}{\beta}\right) R_E} \right]}_{\text{Slope}} V_{CE} + \underbrace{\left[\frac{1}{R_C + \left(\frac{\beta + 1}{\beta}\right) R_E} \right]}_{\text{Intercept with } I_C \text{ axis}} V_{CC}$$

$$\text{Intercept with } V_{CE} \text{ axis} = V_{CC}$$